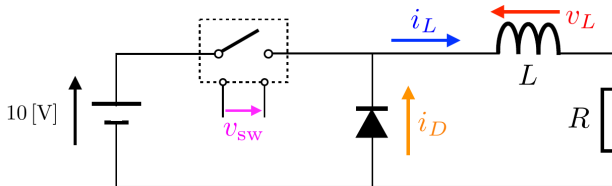


定常状態における降圧チョッパ回路の各波形



$D = 0.5$
 $f_{sw} = 1.0$ [kHz]
 $L = 30$ [mH]
 $R = 10$ [Ω]

教科書P53

