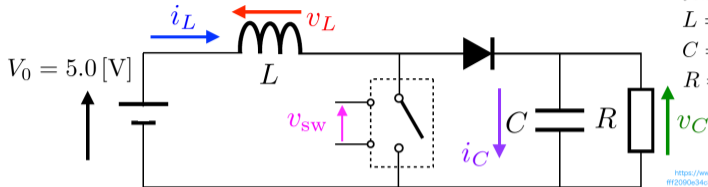


過渡応答時の各素子の振る舞い



$D = 0.583$
 $f_{sw} = 20 \text{ [kHz]}$
 $L = 700 \text{ [}\mu\text{H]}$
 $C = 500 \text{ [}\mu\text{F]}$
 $R = 28.8 \text{ [}\Omega\text{]}$

<https://www.notion.so/source/innoc/f2090e34c86166e583fa43266a2d967?ps=4#f2090e34c86166e583fa43266a2d967>

教科書P71

