
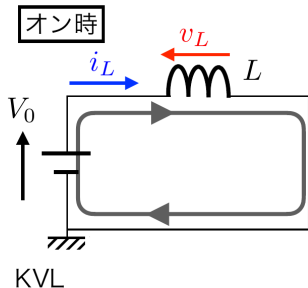


スイッチのオンオフ時にコイルにかかる電圧

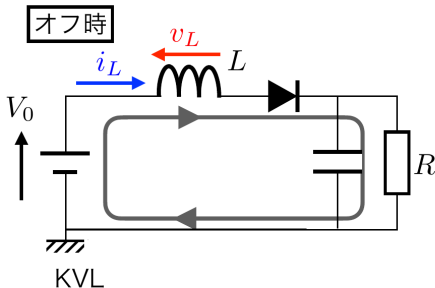

$$V_0 - v_L = 0$$

$$v_L = V_0$$



$$V_0 - v_L - v_C = 0$$

$$v_L = V_0 - v_C$$