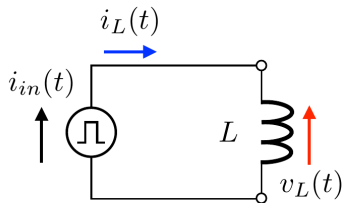


コイルに電流源を繋げてはいけない理由

コイルに電流源を繋ぐとどうなる？



$$v_L(t) = L \frac{di_L(t)}{dt}$$

A callout box pointing to the derivative graph. It contains the expression $L \frac{I_0}{0}$, where I_0 is the peak current of the square wave.

