
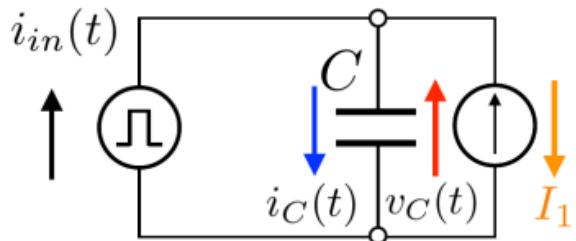


定常状態時の電流の振動の大きさ

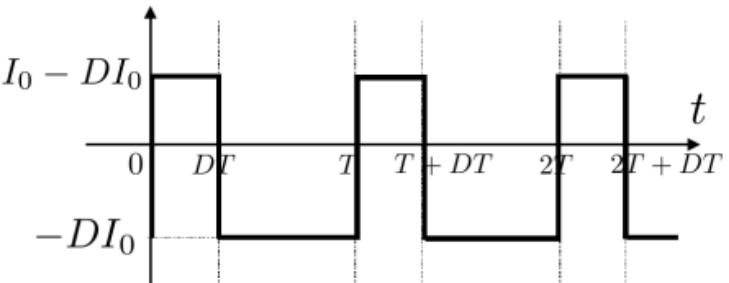


$$i_C(t)$$



$$i_C(t) = C \frac{dv_C(t)}{dt}$$

$$\int_0^{DT} i_C(t) dt = C \int_0^{DT} \frac{dv_C(t)}{dt} dt$$
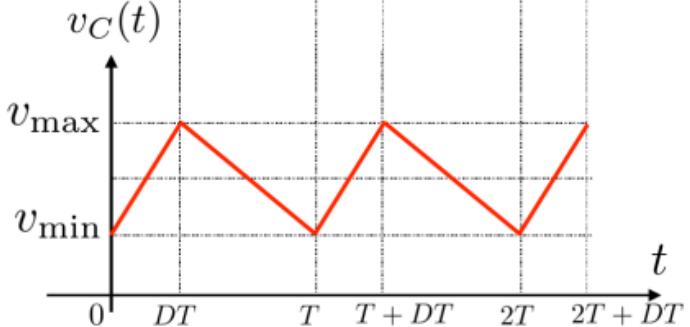
$$\begin{aligned} v_{\max} - v_{\min} &= \frac{1}{C} DT (I_0 - DI_0) \\ &= \frac{DT(1 - D)I_0}{C} \end{aligned}$$



振動を小さくするにはどうすれば良い？